

# Design of a Switched-Capacitor Amplifier

## H05E4a DAMSIC Project 2023

Parts I, II and III: Parameter derivation, Ideal, Symmetrical, Folded and Gain Boosted OTA

Students: Jakov Sola, Simon Pedersen

Group ID: 2

## 1 General Information and Summary

### 1.1 Given Target Specifications

Parameter	Unit	Specification
Sampling Frequency	MHz	50
SNR	dB	45
Static Gain Error	%	0.05
Dynamic Settling Error	%	2.2
Phase Margin (Min.)	deg	60
$C_L$	pF	2
Min. Input Swing	mV <sub>pp</sub>	50
Max. Input Swing	mV <sub>pp</sub>	100
Closed-Loop Gain	V/V	10
Input Pair	-	nmos

### 1.2 Derivation of System Design Parameters

$$C_{FB} = \frac{1}{10} C_{in}$$

$$A_{OL} = \frac{A_{idealCL}(\epsilon_{gain} + 1)}{1 - \beta A_{idealCL}(\epsilon_{gain} + 1)} = \frac{10.005}{1 - \frac{1}{10} 10.005} = -20010$$

$$BW = -\frac{2f_s \ln(\epsilon_{set})}{2\pi} = -2 \times 50 \times 10^6 \times \frac{\ln(0.022)}{2\pi} = 60.7 MHz$$

$$GBW = A_{CL} BW = 10.005 \times 60.7 \times 10^6 = 607 MHz$$

$$G_m = GBW \times 2\pi \times C_{out} \approx GBW \times 2\pi \times C_l = 7.63 mS$$

## 2 Ideal OTA

 


Figure 1 Open loop amplitude response<sup>1</sup>

 
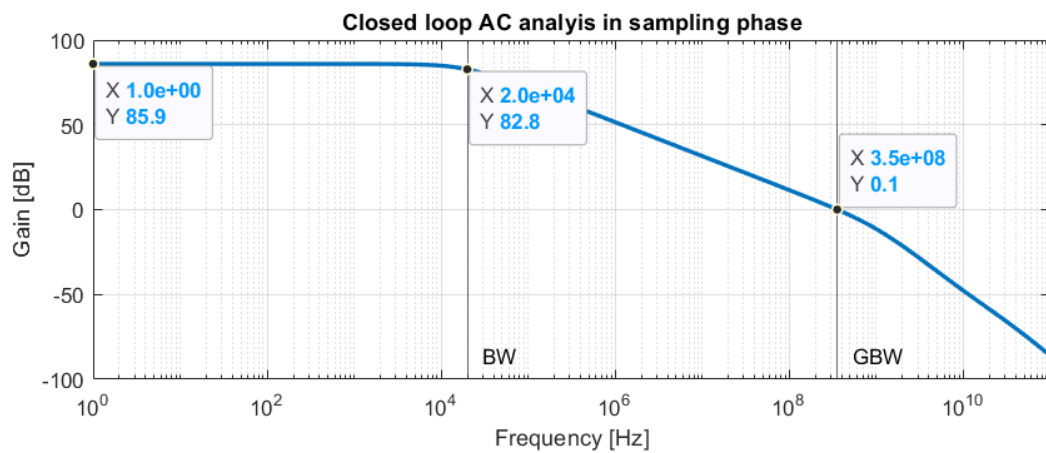


Figure 2 Closed loop amplitude and phase response (sampling phase)

<sup>1</sup> Data tips on all of the plots are dynamically placed to the closest sample point by a Matlab script

 


Figure 3 Transient simulation with  $f_{sw}=f_{in}=50\text{MHz}$

 


Figure 4 Transient simulation with  $f_{sw}=f_{in}=50\text{kHz}$

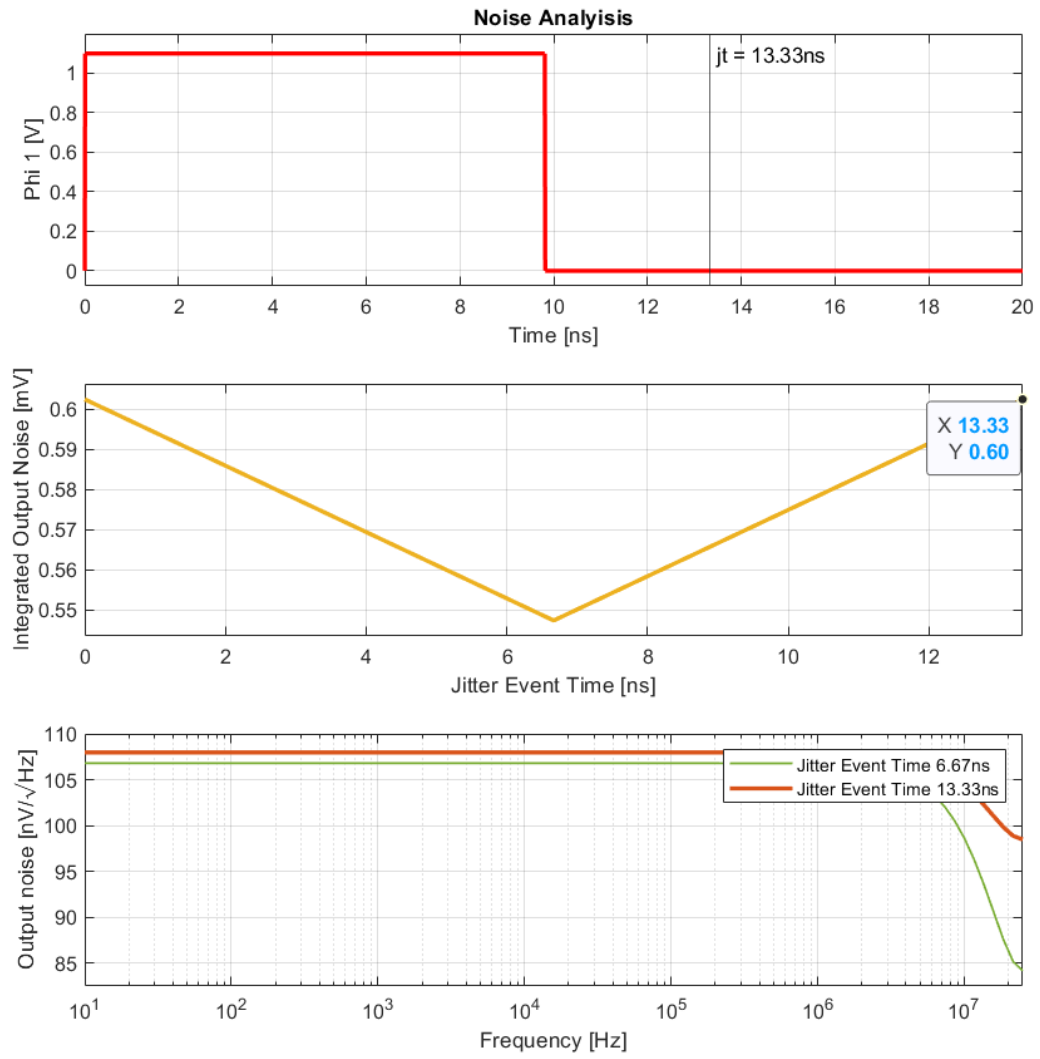



Figure 5 Noise simulation

### 3 Symmetrical OTA

#### 3.1 Table of Achieved Results

Parameter	Unit	Achieved
Input Swing	mV <sub>pp</sub>	<b>100</b>
Output Swing	mV <sub>pp</sub>	<b>964</b>
Total Integrated Output Noise	mV <sub>rms</sub>	<b>3.24</b>
SNR	dB	<b>40.8</b>
C <sub>L</sub>	pF	<b>2</b>
C <sub>FB</sub>	pF	<b>0.23p</b>
C <sub>IN</sub>	pF	<b>2.3p</b>
Open-Loop Gain	dB	<b>53.4</b>
Closed-Loop Gain	V/V	<b>9.64</b>
GBW (Sample Phase)	MHz	<b>630</b>
Phase Margin (Sample Phase)	deg	<b>31</b>
Dynamic Settling Error	%	<b>3.6</b>
Static Gain Error	%	<b>3.3</b>
Power dissipation	mW	<b>2.19</b>

## 3.2 Schematic Design

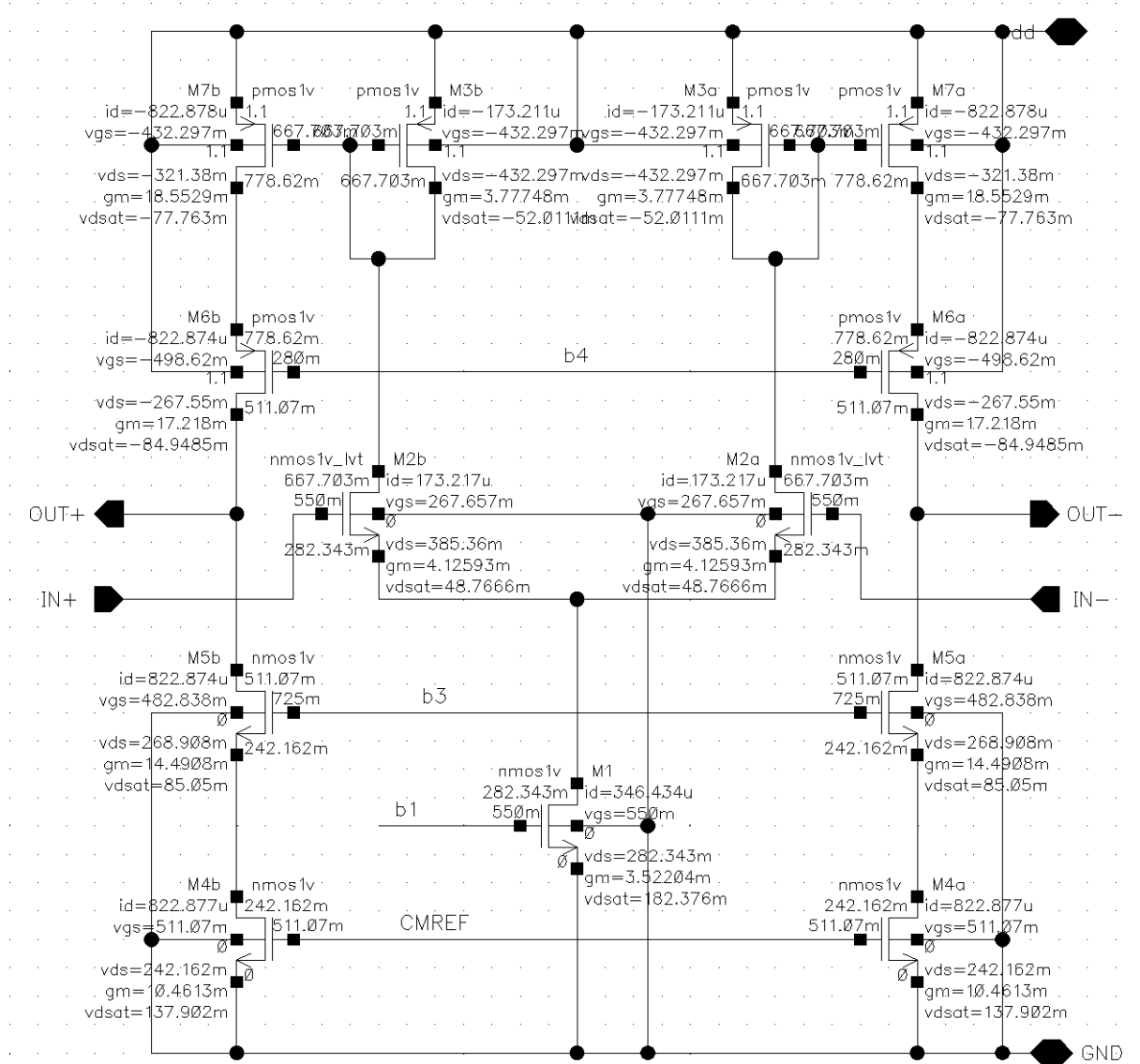

Type	Name	Value	Transistor
Supply	vdd	1.1	
Bias	b1	550m	
	b2	0m	
	b3	725m	
	b4	280m	
	SP	550m	
Tail	Wfn_bias	2u	M1
	bias_n_L	1u	
	bias_n_fn	30	
Input (Low Vt)	Wfn_in_n	2u	M2
	in_n_fn	350	
	in_n_L	45n	
Input mirror	Wfn_in_mirror	2u	M3
	in_p_fn	150	
	in_p_L	45n	
Output nMOS	Wfn_n	2u	M4/M5
	out_n_L	300n	M5
	out_n_fn	150	
	out_n_L_2	600n	M4
	out_n_fn2	80	
Output pMOS	W_fn_p	2u	M6/M7
	out_p_fn	200	M6
	out_p_L	300n	
	out_p_fn2	330	M7
	out_p_L2	200n	
Load	Cl	2p	
CMFB	CMFB_gain	1	
	CMFB_r	10	
	SP	550m	

### 3.3 Simulation Results

 


Figure 6 Open loop amplitude response

 


Figure 7 Closed loop amplitude and phase response (sampling phase)



 


Figure 8 Transient simulation with  $f_{sw}=f_{in}=50\text{MHz}$

 


Figure 9 Transient simulation with  $f_{sw}=f_{in}=50\text{kHz}$

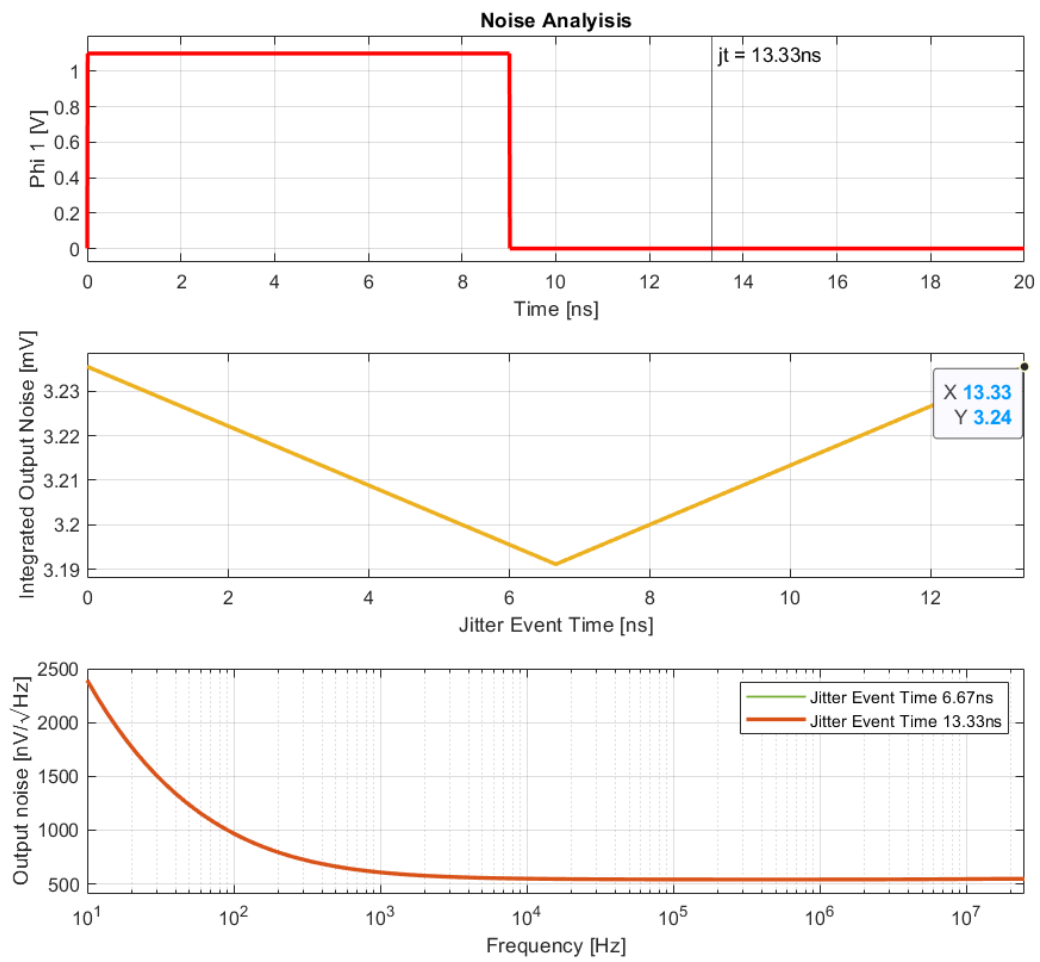


Figure 10 Noise simulation

## 4 Folded cascode OTA

### 4.1 Table of Achieved Results

Parameter	Unit	Achieved
Input Swing	mV <sub>pp</sub>	<b>100</b>
Output Swing	mV <sub>pp</sub>	<b>932</b>
Total Integrated Output Noise	mV <sub>rms</sub>	<b>1.6</b>
SNR	dB	<b>46.9</b>
C <sub>L</sub>	pF	<b>2p</b>
C <sub>FB</sub>	pF	<b>0.5p</b>
C <sub>IN</sub>	pF	<b>5p</b>
Open-Loop Gain	dB	<b>48.3</b>
Closed-Loop Gain	V/V	<b>9.34</b>
GBW (Sample Phase)	MHz	<b>230</b>
Phase Margin (Sample Phase)	deg	<b>82</b>
Dynamic Settling Error	%	<b>10.2</b>
Static Gain Error	%	<b>6.6</b>
Power dissipation	mW	<b>1.98</b>

## 4.2 Schematic Design

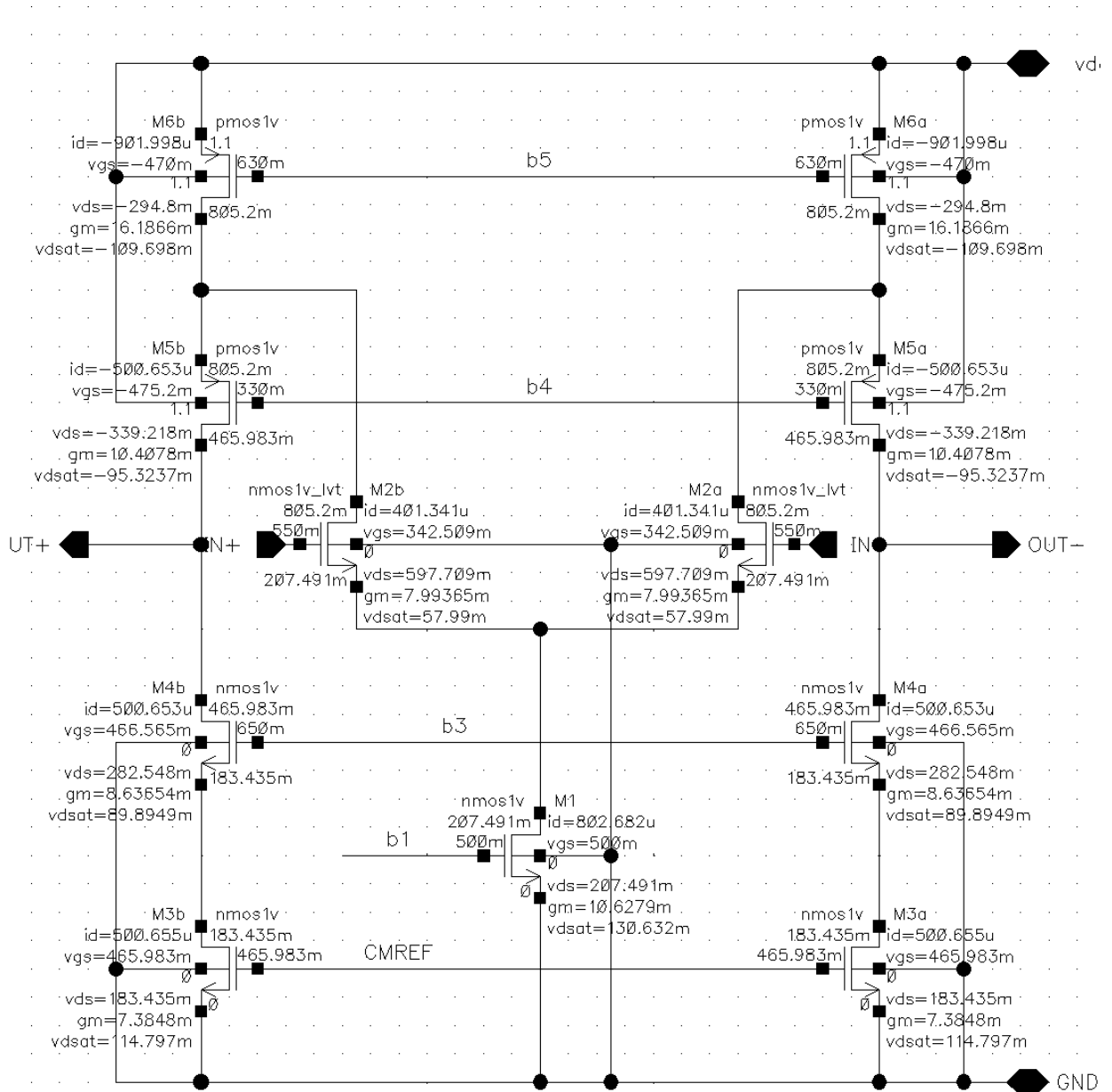


Figure 11 DC Operating point

Type	Name	Value	Transistor
Supply	vdd	1.1	
Bias	b1	500m	
	b2	450m	
	b3	650m	
	b4	330m	
	b5	630m	
	SP	550m	
Tail	Wfn_bias	1.5u	M1
	bias_n_L	600n	
	bias_n_fn	120	
Input (Low Vt)	Wfn_in_n	1.5u	M2
	in_n_fn	160	
	in_n_L	90n	
Output nMOS	Wfn_n	1.5u	M3/M4
	out_n_L	450n	M4
	out_n_fn1	150	
	out_n_L_2	450n	M3
	out_n_fn2	150	
Output pMOS	W_fn_p	1.5u	M5/M6
	out_p_fn	233	M5
	out_p_L	390n	
	out_p_fn2	233	M6
	out_p_L2	450n	
Load	Cl	2p	
CMFB	CMFB_gain	10	
	CMFB_r	1k	
	SP	550m	

### 4.3 Simulation Results

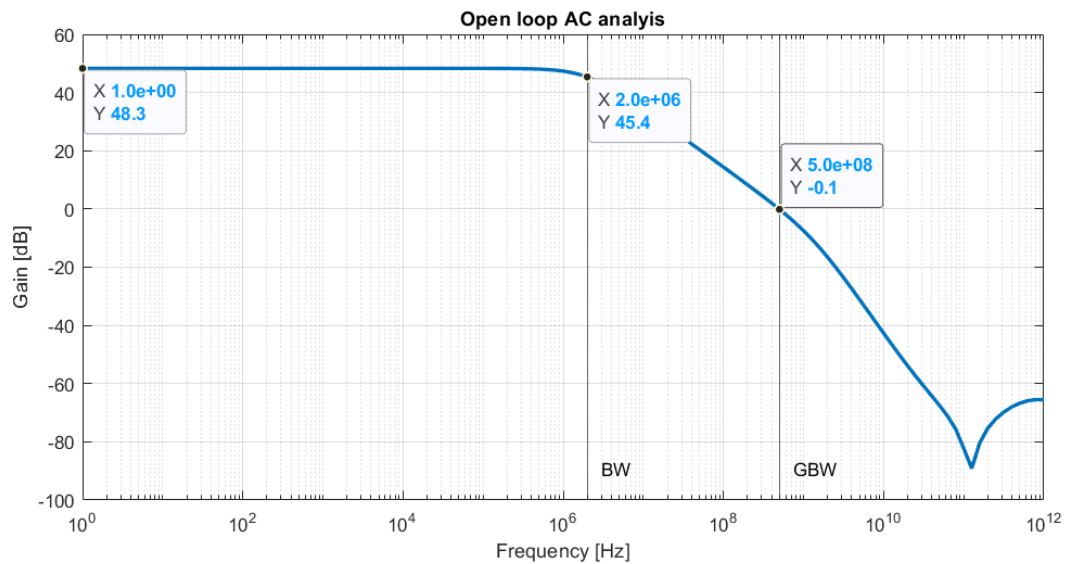


Figure 12 Open loop amplitude response

 


Figure 13 Closed loop amplitude and phase response (sampling phase)

 


Figure 14 Transient simulation with  $f_{sw}=f_{in}=50\text{MHz}$

 


Figure 15 Transient simulation with  $f_{sw}=f_{in}=50\text{kHz}$

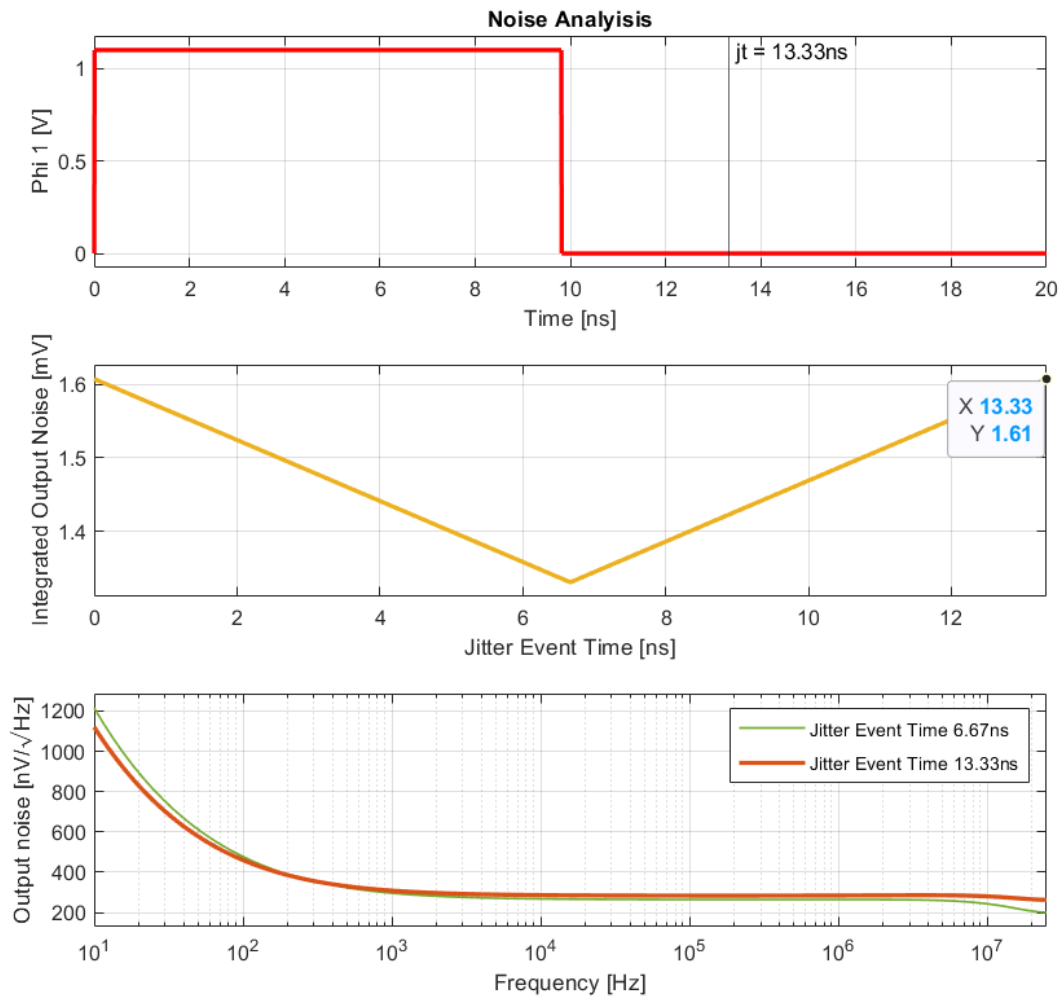


Figure 16 Noise simulation



## 5 Gain-boosted OTA

### 5.1 Table of Achieved Results

Parameter	Unit	Achieved
Input Swing	mV <sub>pp</sub>	<b>50~100</b>
Output Swing	mV <sub>pp</sub>	<b>499.7~999.2</b>
Total Integrated Output Noise	mV <sub>rms</sub>	
SNR	dB	<b>42.5</b>
C <sub>L</sub>	pF	<b>2p</b>
C <sub>FB</sub>	pF	<b>0.8</b>
C <sub>IN</sub>	pF	<b>8</b>
Open-Loop Gain	dB	<b>91.5</b>
Closed-Loop Gain	V/V	<b>9.99</b>
GBW (Sample Phase)	MHz	<b>380</b>
Phase Margin (Sample Phase)	deg	<b>79</b>
Dynamic Settling Error	%	<b>0.7</b>
Static Gain Error	%	<b>0.038 (transient sim); 0.84 (PAC sim)</b>
Power dissipation	mW	<b>8.31</b>

## 5.2 Schematic Design

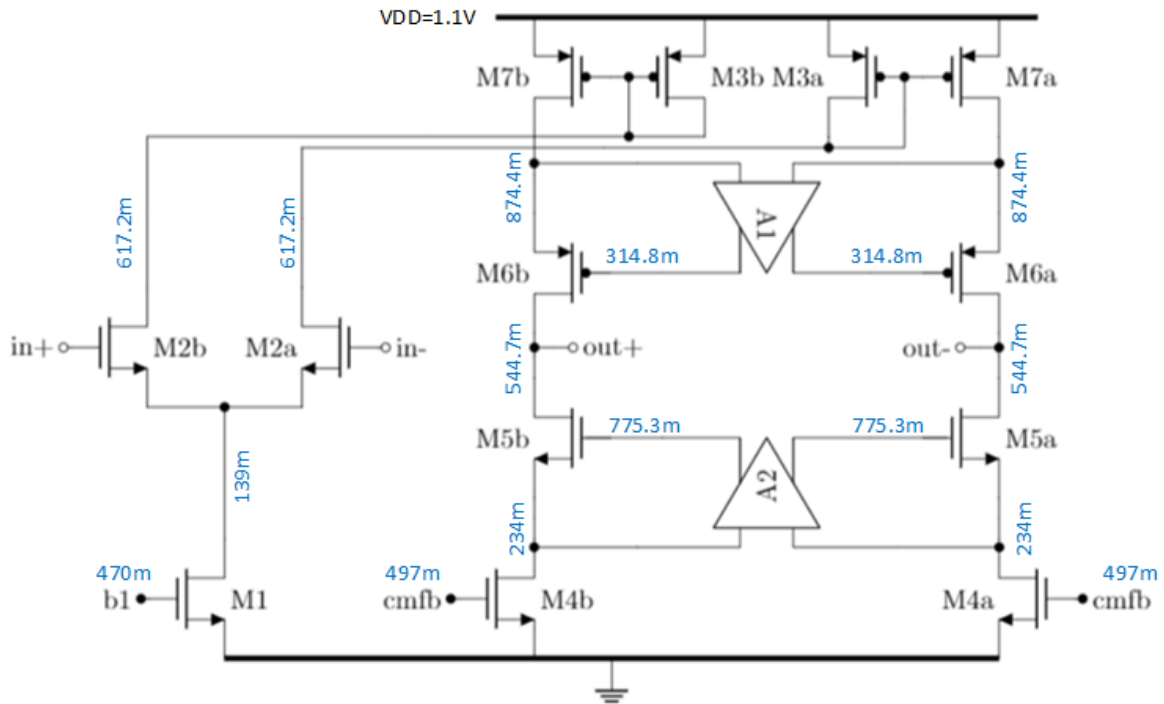


Figure 17 DC Operating point of main OTA

Transistors	Model	Vds[mV]	Vdsat[mV]	gm/Id[S/A]	gm[mS]	Id[mA]
<b>M1</b>	nmos1v	139	116.8	14.3	15.76	1.1
<b>M2</b>	nmos1v_lvt	478.2	61.9	15.1	8.33	0.55
<b>M3</b>	pmos1v_lvt	-452.7	-82.4	13.8	7.59	-0.55
<b>M4</b>	/	235	108	14.8	14.7	11
<b>M5</b>	/	310	102.8	15.17	15	1
<b>M6</b>	pmos1v	-329.7	-98.5	16.3	16.13	-0.99
<b>M7</b>	pmos1v	-225.6	-109.1	17.6	17.4	-0.99

The main OTA is presented with a table due to its size. It is not clearly readable if it is just exported from Cadence.

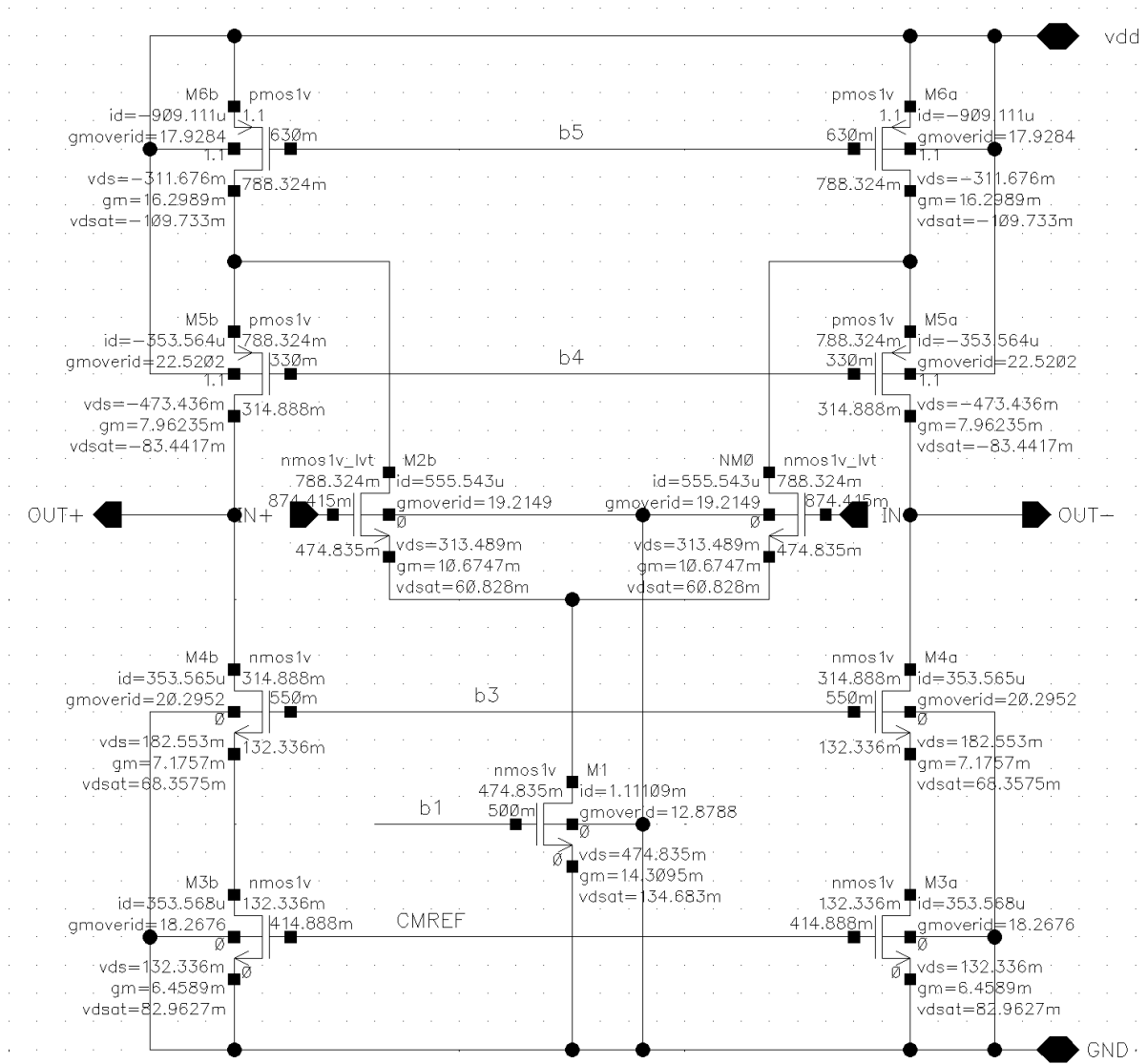


Figure 18 DC Operating point of A1 OTA

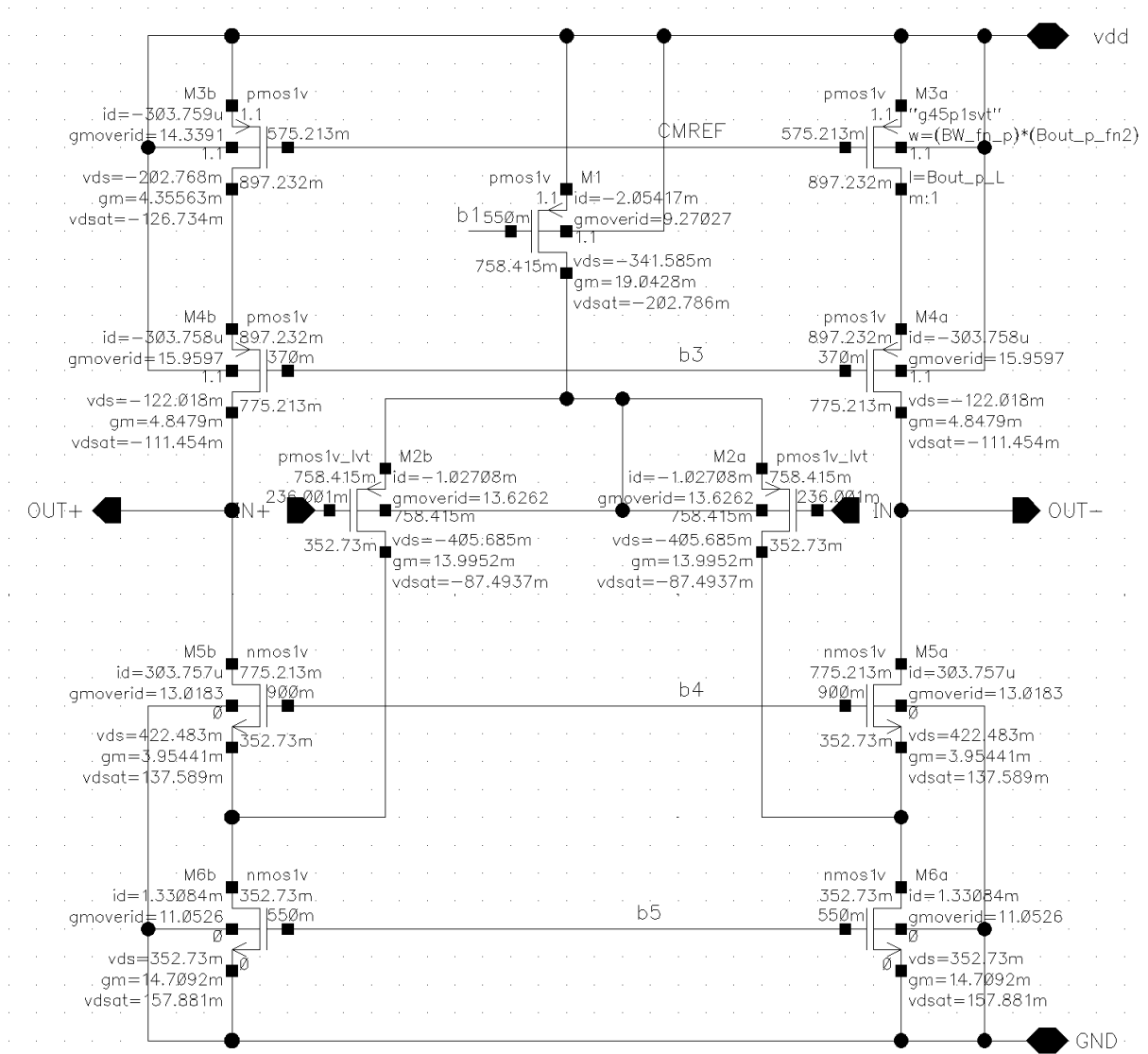


Figure 19 DC Operating point of A2 OTA

Main OTA			
Type	Name	Value	Transistor
Supply	vdd	1.1	
Bias	b1	470m	
Tail	Finger W	1.5u	M1
	Finger #	420	
	L	1.1u	
Input nMOS (Low Vt)	Finger W	1.5u	M2
	Finger #	53	
	L	45n	
pMOS (Low Vt)	Finger W	1.5u	M3
	Finger #	27	M3
	L	45n	M3
Output nMOS	Finger W	1.5u	M4/M5
	Finger #	100	M5
	L	215n	
	Finger #	133	M4
	L	340n	
Output pMOS	Finger W	1.5u	M5/M6
	Finger #	100	M5
	L	110n	
	Finger #	200	M6
	L	300n	
CMFB	Gain	10	
	R	10	
	CMFB SP	550m	

Gain Boosting nMOS input OTA – A1			
Type	Name	Value	Transistor
Supply	vdd	1.1	
Bias	b1	500m	
	b3	550m	
	b4	330m	
	b5	630m	
Tail	Finger W	1.5u	M1
	Finger #	144	
	L	600n	
Input (Low Vt)	Finger W	1.5u	M2
	Finger #	192	
	L	90n	
Output nMOS	Finger W	2u	M3/M4
	Finger #	200	M4
	L	450n	
	Finger #	200	M3
	L	450n	
Output pMOS	Finger W	1.5u	M5/M6
	Finger #	233	M5
	L	390n	
	Finger #	233	M6
	L	450n	
CMFB	Gain	1	
	R	10	
	CMFB SP	315m	

Gain Boosting pMOS input OTA – A2			
Type	Name	Value	Transistor
Supply	vdd	1.1	
Bias	b1	550m	
	b3	370m	
	b4	900m	
	b5	550m	
Tail	Finger W	1.5u	M1
	Finger #	300	
	L	1u	
Input (Low Vt)	Finger W	1.5u	M2
	Finger #	50	
	L	45n	
Output nMOS	Finger W	1.5u	M5/M6
	Finger #	40	M5
	L	600n	
	Finger #	60	M6
	L	400n	
Output pMOS	Finger W	1.5u	M3/M4
	Finger #	30	M4
	L	200n	
	Finger #	50	M3
	L	200n	
CMFB	Gain	1	
	R	10	
	CMFB SP	775m	

### 5.3 Simulation Results

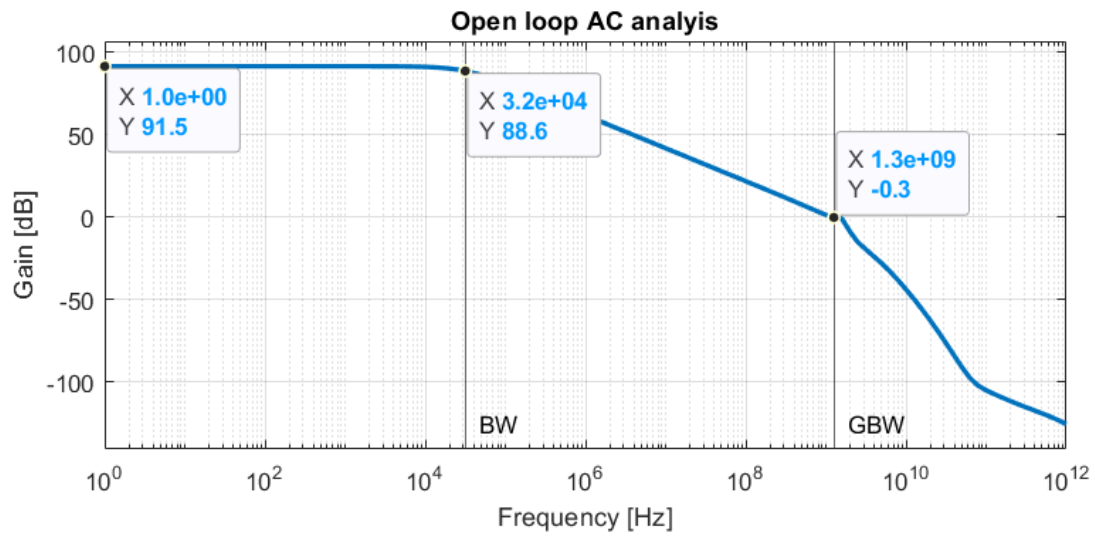


Figure 20 Open loop amplitude response

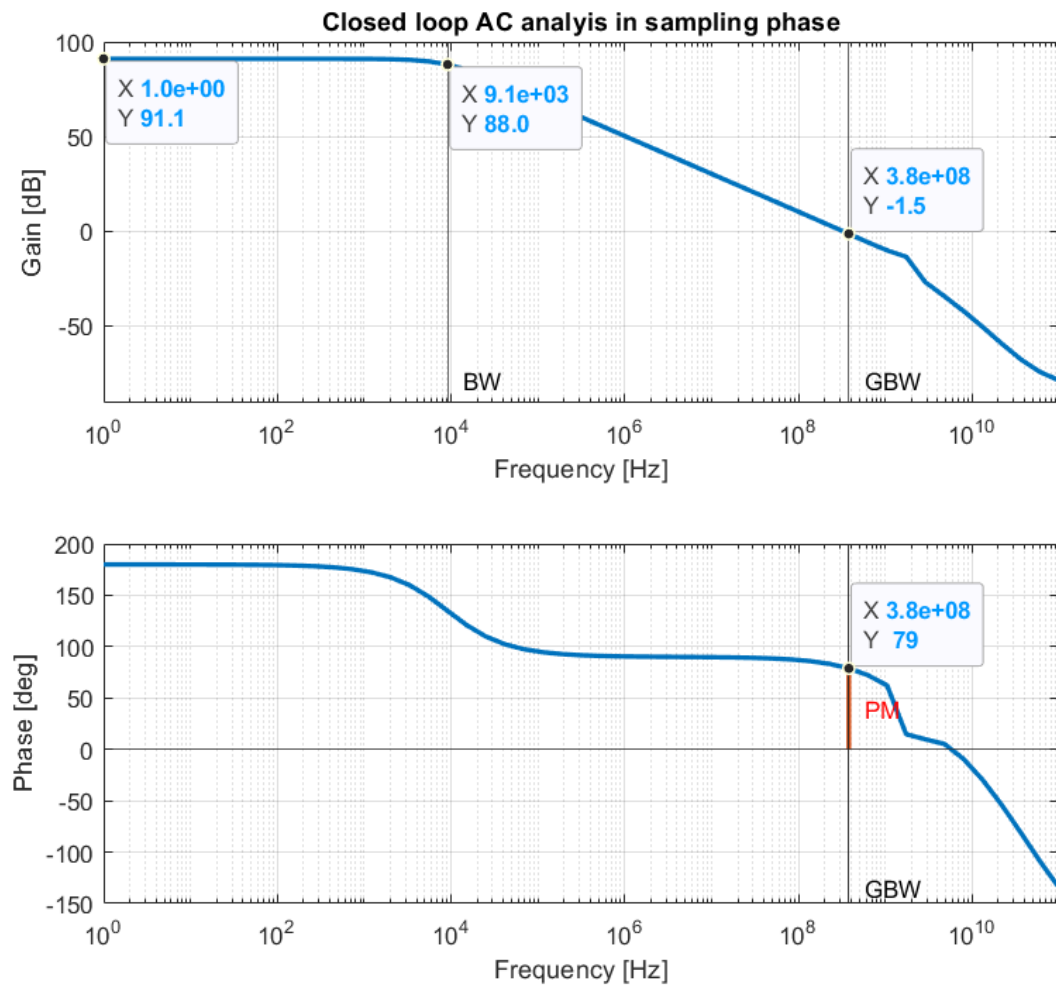


Figure 21 Closed loop amplitude and phase response (sampling phase) - differential loop

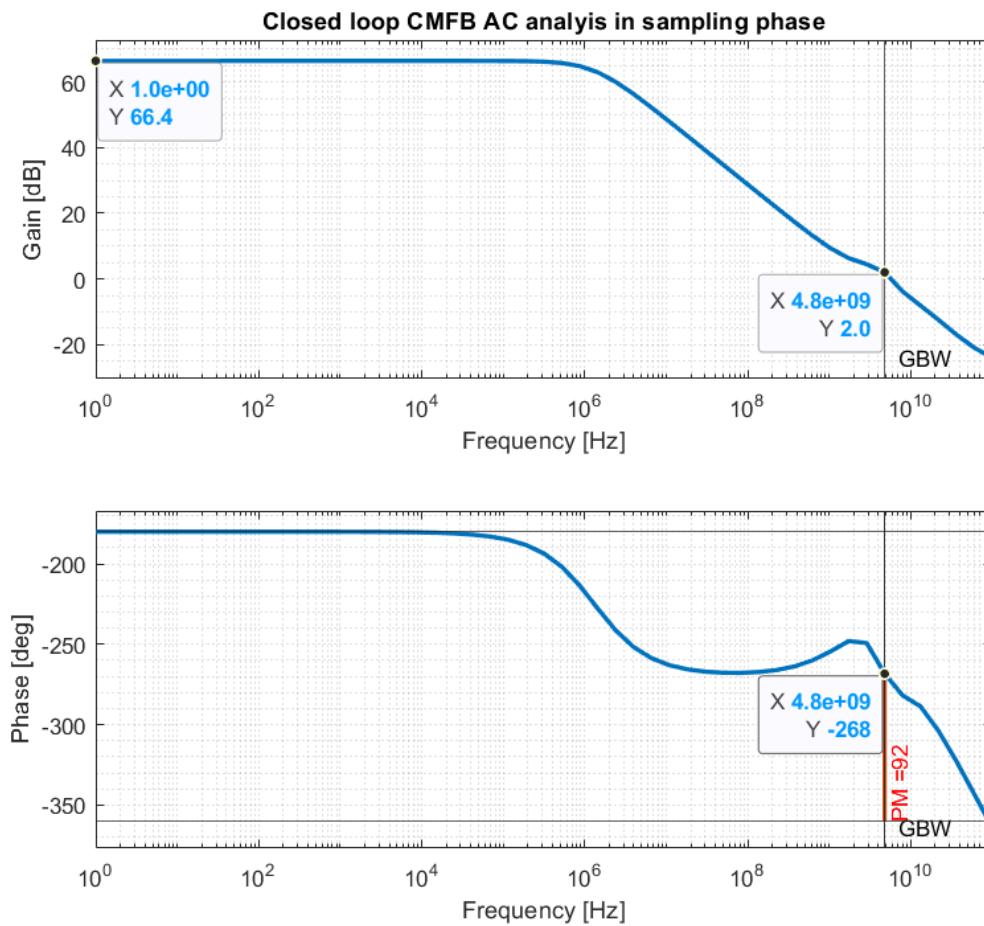


Figure 22 Closed loop amplitude and phase response (sampling phase) – CMFB loop

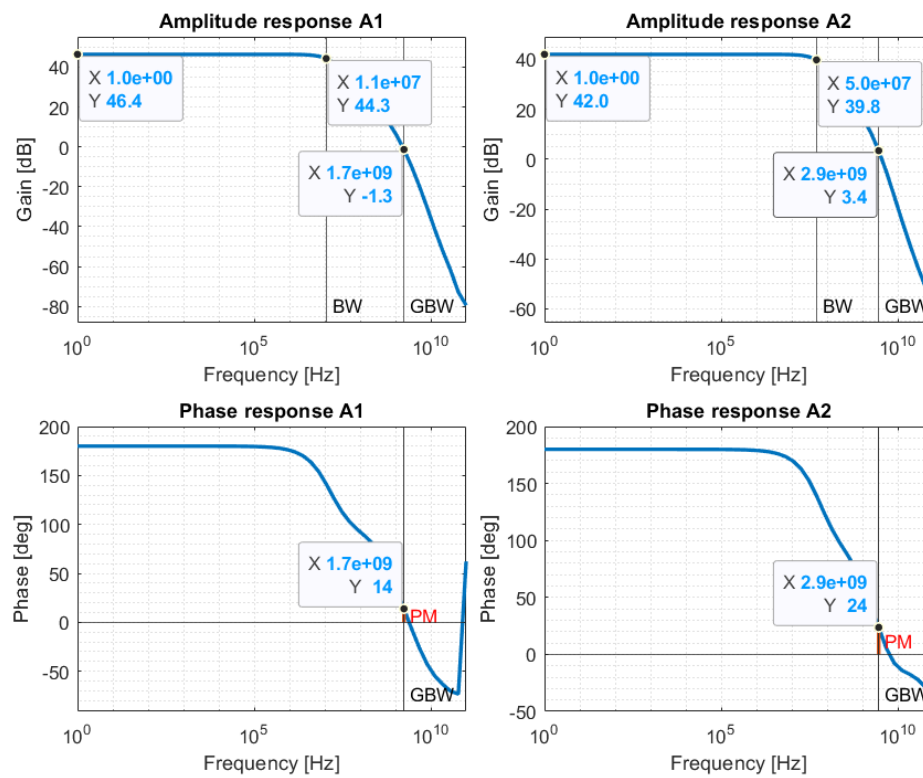


Figure 23 Closed loop amplitude and phase response A1 and A2



 


Figure 24 Transient simulation with  $f_{sw}=f_{in}=50\text{MHz}$

 


Figure 25 Transient simulation with  $f_{sw}=f_{in}=50\text{kHz}$


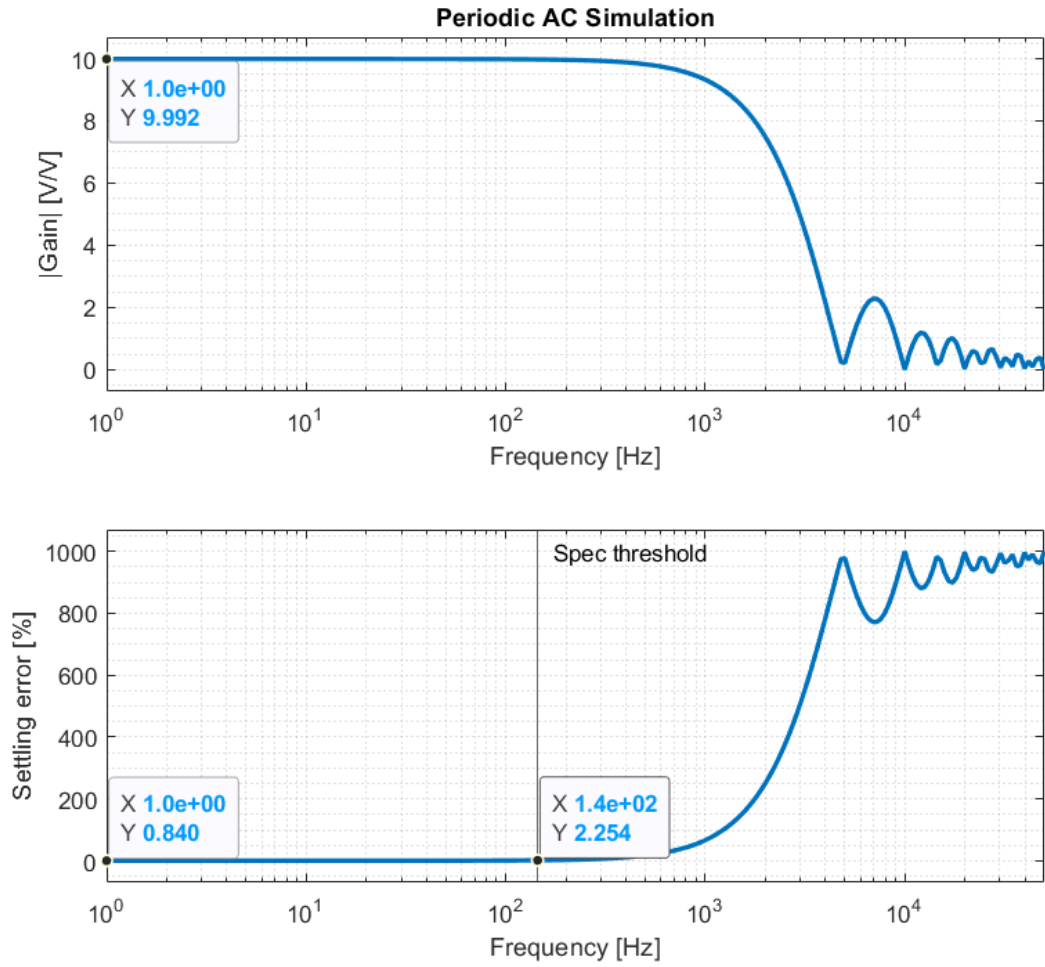


Figure 26 Closed loop PAC simulation

 

## 6 Summary and Additional Remarks

### Specifications


- We managed to reach all of the given specifications except the SNR that is 2.5dB less than required. We were **able to meet all the specifications** when using voltage sources to adjust the CM output of the gain boosting amplifiers. Our dynamic settling error (0.7%) is significantly better than the specification (2.2%). According to the PAC simulation we do not meet the static gain error specification but do in the transient simulation.

### Plotting and specification extraction

- We wrote a script in Matlab that takes in CSV data from Cadence, analyses it and plots the results. It automatically adjusts the axis scales, calculates important points such as the BW, GBW, phase margin and dynamically labels them on the plots in a clear and readable way. This eliminates the time-consuming task of the user having to manually place points on the graph and makes the graphs and the important points easier to read.
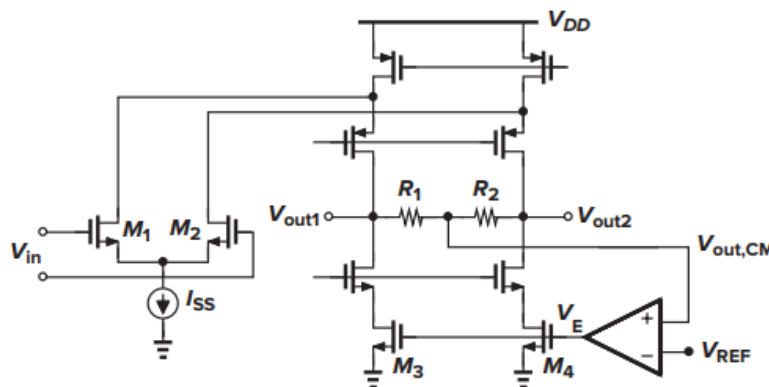
## 7 Other Results

- We attempted to make a real CMFB block instead of using the ideal one that was provided to us. We managed to implement the following topology by making a separate simple OTA that would be used as a comparator in the feedback loop. This gave stable and good results when used only on the folded cascode OTA but was very unstable in the gain boosting implementation due to too much gain.



- An obvious downside of this implementation are the two sensing resistors that cause many problems. We had planned to replace them with a better CM sensing circuit later on.